
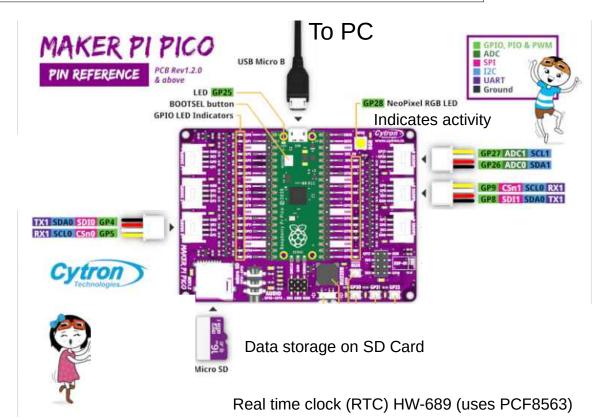
## Temperature Logger Concept with Maker Pi Pico Rob Probin, Dec 2022



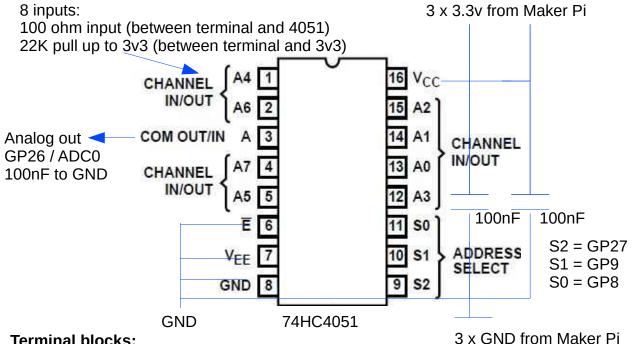SCL to GP5 SDA to GP4 GND to GND Vcc to 3v3





**Terminal blocks:** 

2 inputs to 1 shared GND

20K NTC Thermocouples go between input and ground.